

## Characteristics of an ideal op-Amp :-

- The important characteristics of an ideal op-Amp, are as follows:
- 1. Infinite voltage gain ( $A_v = \infty$ ): - The open loop gain of an ideal op-Amp is denoted by  $A_v$ .

The value of  $A_v$  for an ideal op-Amp is  $\infty$ .

### 2. Infinite input resistance ( $R_i = \infty$ )

Input resistance is the total resistance measured b/w the two input terminals of op-Amp.

Due to this, the current flowing in each input terminal will be zero i.e.  $I_{B1} = I_{B2} = 0$

### 3. Zero output resistance ( $R_o = 0$ )

The output resistance of op-Amp is the resistance viewed from its output terminal.

The output resistance of an ideal op-Amp is zero.

### 4. Zero offset voltage.

The voltage which is produced at the output when both input voltages ( $V_1 = V_2 = 0$ ) are zero is called offset voltage.

This means that for an ideal op-Amp output voltage is zero when input voltage is zero.

### 5. Infinite Bandwidth:-

Bandwidth of an amplifier is the range of frequencies over which all the signal frequencies are amplified almost equally.

The bandwidth of an ideal op-Amp is  $\infty$  so it can amplify any frequency signal from 0 to  $\infty$  Hz.

### 6. Infinite CMRR:-

The CMRR is the ability of op-Amp to reject common mode signal successfully.


$$\text{CMRR} = \frac{|A_v|}{|A_e|}. \text{ For an ideal op-Amp CMRR is } \infty \text{ so that } A_e = 0$$

### 7. Infinite slew rate ( $S = \infty$ )

Slew rate is defined as the maximum rate of change of output voltage with time i.e.  $S = \frac{dv_o}{dt} \text{ max.}$   $v_o = A_v v_d, A_v = \infty \text{ for open loop gain.} \therefore v_o = \infty,$   
 $\text{so, } S = \frac{dv_o}{dt} \text{ max.} = \infty.$

For an ideal op-Amp, slew rate is  $\infty$ .

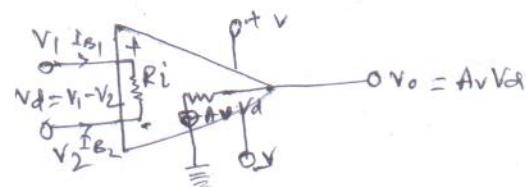However, a practical op-Amp deviates from these ideal characteristic. For exm., IC op-Amp - 741, open loop voltage gain  $\approx 2 \times 10^5$ , input impedance  $\approx 2 M\Omega$ , output impedance  $\approx 75 \Omega$ , unity gain freq.  $\approx 1 \text{ MHz}$  and input offset voltage  $\approx 1 \text{ mV}$ .




Equivalent circuit diagram of an ideal op-Amp.

## Operational Amplifier:-


- The term Op-Amp stands for "Operational Amplifier".
- An Op-Amp is a high gain ( $10^5$ - $10^6$ ) amplifier which is used to perform variety of operations such as amplification, addition, subtraction, differentiation, integration etc.
- Advantages of Op-Amp over conventional amplifier:
  - It has smaller size
  - It has less power consumption
  - It is easy to replace
  - Low cost.
  - High reliability.

### Symbol & terminals:-

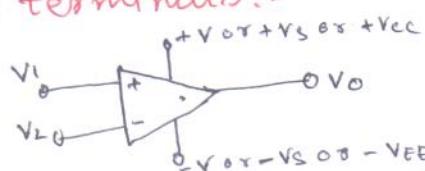

An op-Amp has atleast following 5 terminals:

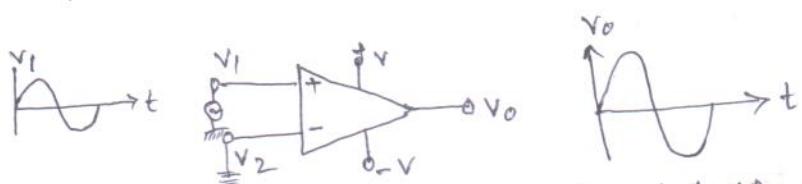- The non-inverting input terminal marked as '+'.
- The inverting input terminal marked as '-'.
- The positive supply voltage  $+V$ .
- The negative supply voltage  $-V$ .
- The output terminal  $V_O$ .



- If we connect the input signal to the non-inverting terminal, then the amplified output signal is in phase with the input signal as shown in fig.

- If we connect the input signal to the inverting terminal, then the amplified output signal is  $180^\circ$  out of phase w.r.t the input signal as shown in fig.

